

# EE313 Analog Electronic Laboratory

## 2017-2018 Fall Term Project

### FMCW Based Distance Measuring System

1<sup>st</sup> Halil TEMURTAS 2094522 [halil.temurtas@metu.edu.tr](mailto:halil.temurtas@metu.edu.tr)  
 2<sup>nd</sup> Erdem TUNA 2167419 [erdem.tuna@metu.edu.tr](mailto:erdem.tuna@metu.edu.tr)

**Abstract**—Design of a Frequency Modulated Continuous Wave (FMCW) Based Distance Measuring System

**Index Terms**—component, formatting, style, styling, insert

#### I. INTRODUCTION

Design of a Frequency Modulated Continuous Wave (FMCW) Based Distance Measuring System Aim: In this project, you are going to design a distance measurement system as depicted in Figure 1.

#### II. TRANSMITTER

##### A. Voltage Controlled Oscillator

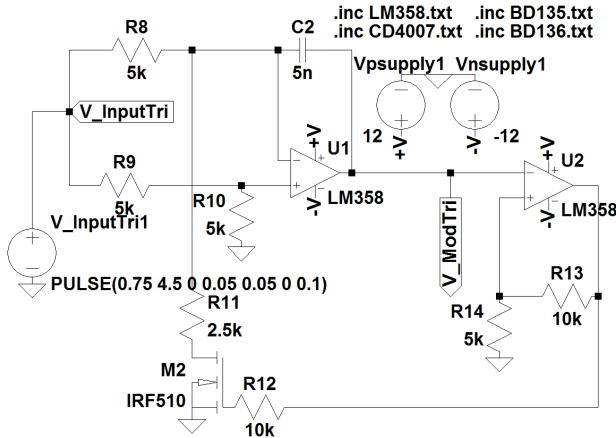


Figure 1: The Voltage Controlled Oscillator Circuit.

Voltage controlled oscillator (VCO) is a circuit that basically maps certain voltage values at the input to a frequency at the output. In other words, VCO outputs different frequencies as the voltage value of the input changes. The circuit to be used as VCO in this project can be seen in Figure 1. To utilize from this mapping property of the VCO in a radar application, the input to the circuit is a triangular wave such that input voltage changes continuously. Essentially,  $R_1$  and  $C_1$  in Figure 1 are the determinative components of the voltage-to-frequency mapping. The  $M_1$  acts like a switch that is ruling the current through the  $C_1$ . The  $V_{ModTri}$  is the frequency modulated output of the circuit. This output will be used in the rest of the project. However,  $V_{ModTri}$  goes one more step in the VCO circuit which is a Schmitt Trigger represented with LM2

opamp. With the positive feedback, LM2 outputs either  $+V$  or  $-V$ . The output of the LM2 effects the state of  $M_1$  with the input triangular voltage.

##### B. Power Amplifier and Speaker

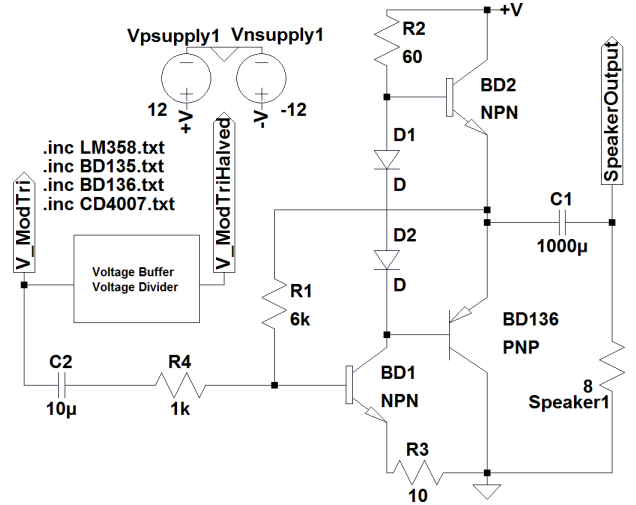


Figure 2: Power Amplifier Circuit Driving the Speaker.

The purpose of this part is to send modulated triangular signal to the electret microphone via a speaker. The circuit is presented in Figure 2. The amplifier is composed of one common emitter with degeneration and a cascode. The amplifier isn't designed to amplify the voltage but the current so that speaker can be driven. The cascode stage increases the bandwidth of the circuit. Also there are feedbacks in all transistors, namely  $BDN_1$ ,  $BDN_2$  and  $BDP_1$  to increase the voltage swing. Lastly speaker is driven with sufficiently large voltage and current values.

#### III. RECEIVER

##### A. Microphone & Microphone Driver

To receive the sound signal coming from the speaker and turn it into an electrical signal, some kind of speaker should be used. For this purpose, an electret microphone will be used.

To drive the electret microphone, a driver circuit will be designed. The design should include feeding for the transistor inside the microphone and amplify the output signal since the

output signal would be too small to be used. But before going amplifying the signal, we shall remove possible dc offsets and noises by a passive high pass filter. The designed driver can be seen at *Figure 3*.

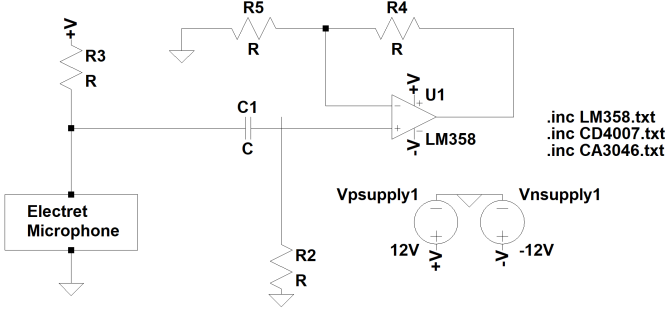


Figure 3: Driver Circuit for Electret Microphone

With simple node analysis in the frequency domain, the cutoff frequency of the passive high pass filter can be found as

$$f_c = \frac{1}{2\pi R_2 C_1}$$

If we take  $R_2 = 10k\Omega$  and  $C_1 = 0.1\mu F$ , cutoff frequency  $f_c$  can be found as

$$f_c = \frac{1}{2\pi * 10 \text{ k}\Omega * 0.1 \mu F} \approx 159Hz$$

This frequency is pretty good for blocking DC offset and noise.

### B. Mixer

Mixer is the device that accepts two input signals and gives a output signal that consists of two distinct signals with different frequencies. While, one of these signals has a frequency that is equal to the difference between the frequencies of first signal and second signal, other signal has a frequency that is summation of the frequencies of first and second signal. In other words, if we assume input signal 1 has a frequency  $f_1$  and input signal 2 has a frequency  $f_2$ . The output would look like

$$O/P \text{ Signal} = A(f_1 + f_2) + B(|f_1 - f_2|)$$

where A and B are the signals having frequencies

$$f_A = f_1 + f_2 \text{ \& } f_B = |f_1 - f_2|$$

respectively.

We know that the distance between source and receiver causes a time delay proportional to the distance for the received signal in comparison to the received signal. Thanks to triangular wave used at the very beginning of the project, the distance between the source and receiver is also proportional to the frequency difference between original source signal and received signal by receiver. This can be understood from the basic principle of VCO. Assume that the first signal left

the VCO and entered the mixer at Time 0 and has a frequency  $f_1$  proportional to the magnitude of triangular wave at Time 0. Similarly second signal entered the Mixer at Time 1 and has a frequency  $f_2$  proportional to the magnitude of triangular wave at Time 1. One period of the input triangular wave and "Time 0" & "Time 1" on top of it can be seen at *Figure 4*.

Therefore, the time shift " $Time 1 - Time 0$ " is proportional to the " $|f_2 - f_1|$ ". Thus, if we can find the frequency difference between this signal, we can easily find the desired distance since the distance can be found by

$$d = (Time 1 - Time 0) * v_s = K * |f_1 - f_2|$$

where K is a constant and  $v_s$  is the speed of sound.

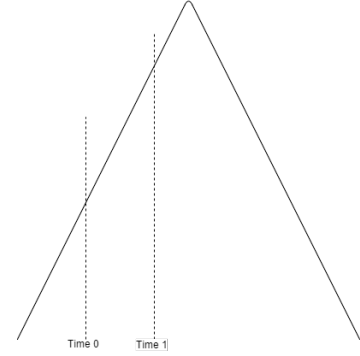


Figure 4: One Period of Triangular Wave

For that purpose, a mixer circuit is what we need and a basic mixer circuit we are planning to use can be seen at *Figure 5*.

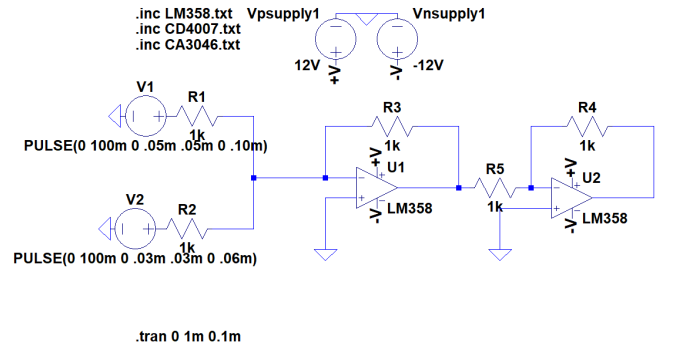


Figure 5: A Multiplier Circuit

### C. Low Pass Filter

Unfortunately, the output signal of mixer does not only carry the frequency difference info but also frequency summation info. Since we are interested with the difference between the frequencies only, a low pass filter should be used to extract the wanted signal.

Low Pass Filters are the type of filters that passes and amplifies the signals having the frequencies lower than the desired frequencies also known as the cut-off frequencies of the filter. Other signals having higher frequencies would be eliminated at the output of the low pass filter.

A basic second order low-pass filter that we are going to use can be seen at Figure 6

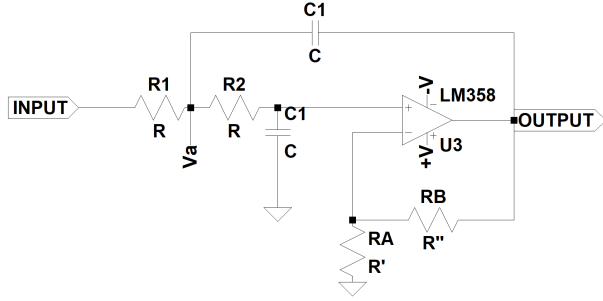


Figure 6: A Second Order Low-Pass Filter

### IV. GENERAL DIAGRAM

General diagram of the project can be seen at Figure 7.

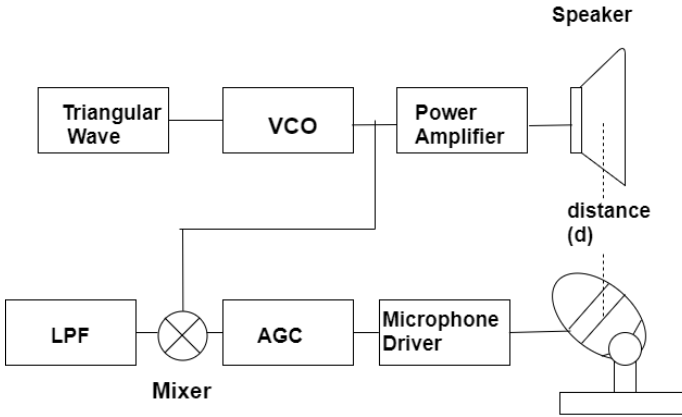


Figure 7: General Diagram of the Project

### V. CONCLUSION

First, a triangular voltage is generated with varying frequencies by a VCO circuit and 10 Hz triangular wave input. Then modulated triangular wave is sent to microphone by a speaker and to mixer at the same time. The microphone transmits the captured signal to the mixer. In the mixer, there are two equivalent inputs but with a phase shift. Output of the mixer is basically sum of two waves having frequencies  $(f_1 + f_2)$  and  $(|f_1 - f_2|)$  that are frequencies of two inputs of the mixer. If this signal is low-passed, the filtered signal have  $(|f_1 - f_2|)$  frequency. By measuring  $(|f_1 - f_2|)$ , the distance between the speaker and the microphone can be found by a simple algebra,  $K * (|f_1 - f_2|)$  where K is a constant to be determined and having unit of  $\frac{\text{Meter}}{\text{Hertz}}$ .